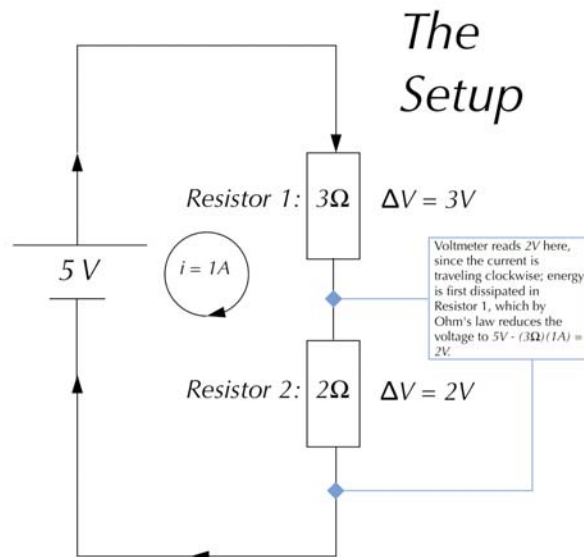


Question #363


This week we venture into world of circuits for a voltage paradox.

Below is a DC circuit with a 5V battery, 3 Ω - and 2 Ω -resistor. The current is flowing clockwise, and a voltmeter (in blue) reads 2V. Click on the image below to view the circuit in more detail.



Now, consider the battery reversed, so that current is instead flowing the counter-clockwise direction.

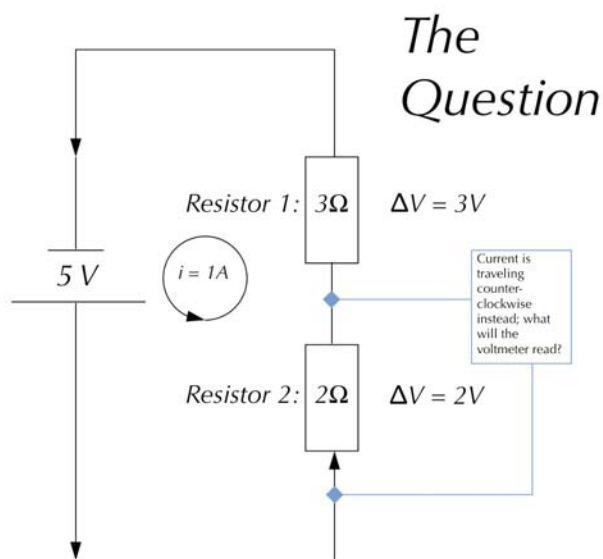Question: What will the voltmeter read now?



- (a) The voltmeter will read -2V, indicating the change in current.
- (b) The voltmeter will read 3V, since the current is traveling counter-clockwise instead; energy is first dissipated in Resistor 2, which by Ohm's law reduces the voltage to $5V - (2\Omega)(1A) = 3V$.
- (c) The voltmeter will still read 2V, because current *actually* flows in the other direction (electrons are negative); nothing has changed.
- (d) Other (you must explain).

Remember, the true test of understanding is when you can dismiss other, plausible conclusions using physics-based reasoning -- not simply getting the "right" answer.

Click here for [Answer #363](#) after February 22, 2010.

[Question of the Week](#)


[Outreach Index Page](#)

[Lecture-Demonstration Home Page](#)



For questions and comments regarding the *Question of the Week* contact [Dr. Richard E. Berg](#) by e-mail or using phone number or regular mail address given on the [Lecture-Demonstration Home Page](#).

The Setup

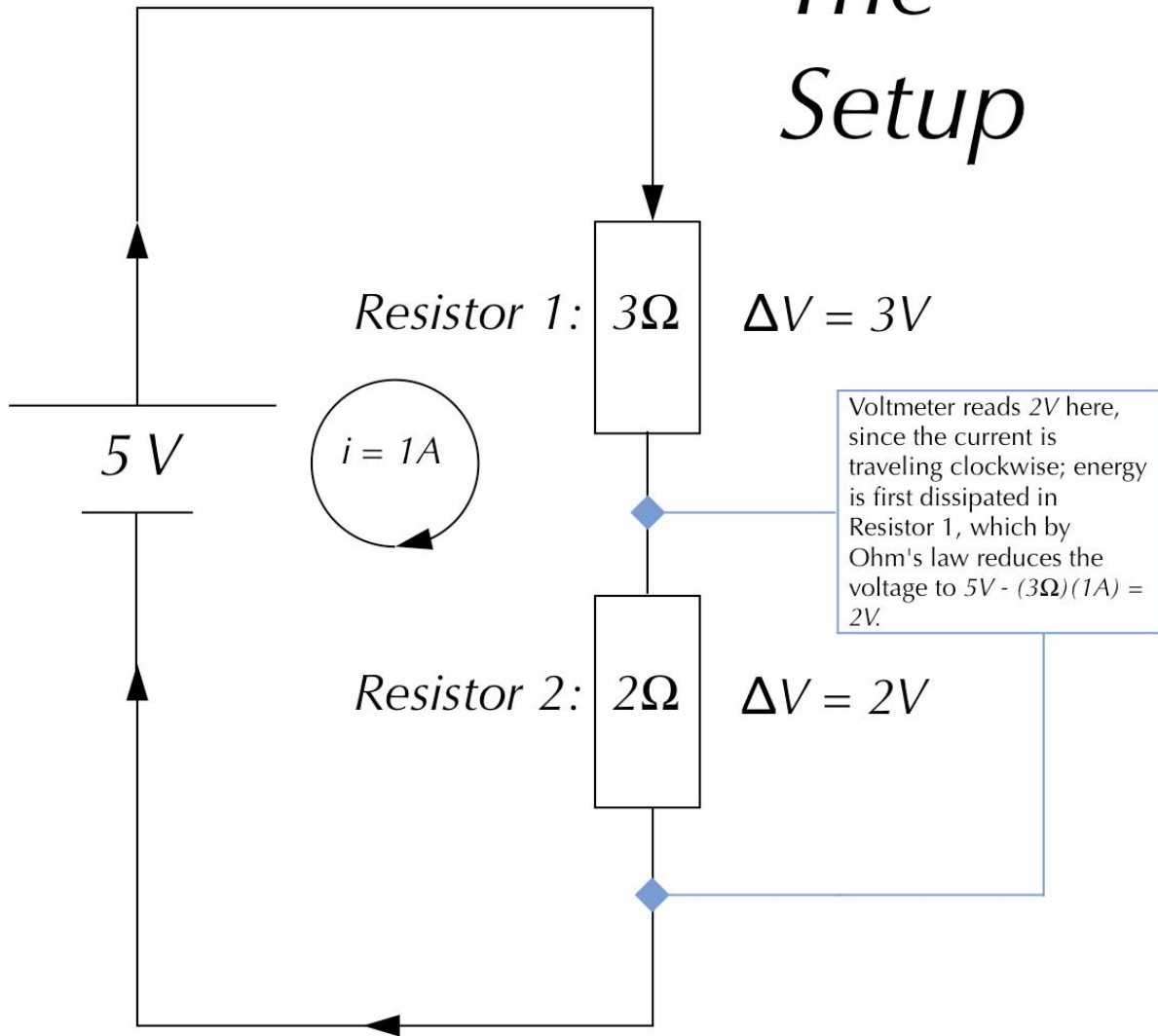

The Question

